



Assignment No -3

Create Schematic Diagram of Rock-chip AP6356S WIF/BT Module;

Datasheet Link:

https://rockchip.fr/ampak/AP6356_datasheet_V1.0_07252014.pdf

Follow this Designing Steps if you Want:

- 1- If any components is not available on EsteemPCB SOM Library,
(Don't create it from scratch try to look into following websites
Snapeda, Ultralibrarian, Components Search Engine)
- 2- Follow the Instructions I have given on DAY-5 for schematic;
- 3- On Power Supply pins use Some 10Uf(0603), 100Nf(0201) Caps.
- 4- In case of any doubt put your question on WhatsApp group.

Note: Please send your complete Assignment on

esteempcb.info@gmail.com with Subject: Assignment no. XX_Your
Name_SOM Course.